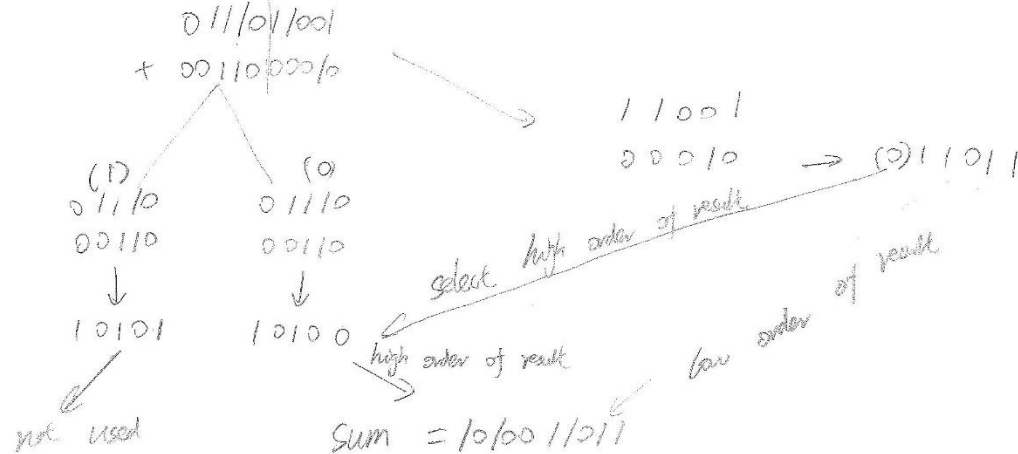


Homework 3 Solutions

1. [Self Study]

a) 10-bit Carry Select Adder: $0111011001 + 0011000010$





b) 10-bit subtraction circuit: $0111011001 - 0011000010$


$$\begin{aligned}
 &0111011001 - 0011000010 \\
 &= 0111011001 + (1100111101) + 1 \\
 &= 0111011001 + 1100111110 \\
 &\quad 0111011001 \\
 &+ 1100111110 \\
 &\hline
 &1010010111
 \end{aligned}$$

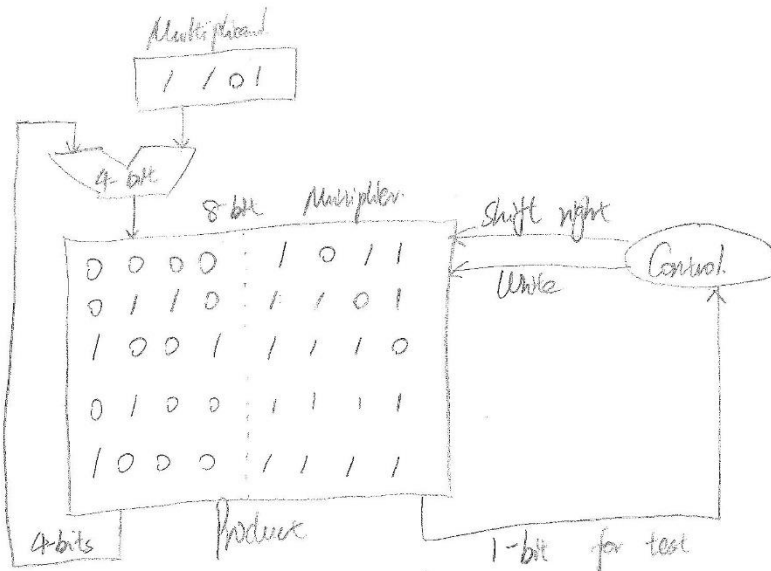 c) 4-bit multiplication -- do for "pencil-and-paper" on both multiply circuits (3.4 and 3.6): 1101×1011


$$\begin{array}{r}
 \text{SS2)} \quad 1101 \quad \text{multiplicand} \\
 \times 1011 \quad \text{multiplier} \\
 \hline
 1101 \\
 1101 \\
 0000 \\
 1101 \\
 \hline
 10001111
 \end{array}$$



 d) "unrolled" 4-bit multiplier: 1101 x 1011



 - e) Carry-Save-Adder (CSA) based 4-bit multiplier -- do for both "pencil-and-paper" and the circuit (the scan from Kavanagh).



2. [Carry Select Adders]

a) Delay = $2*k + 2*(j-2)$, where k = bits of RCA, j = number of blocks
 Delay = $2*4 + 2*(2-2) = 8+0 = 8$

b) Delay = $2*k + 2*(j-2)$, where $k = 4$, $j=3$
 Delay = $2*4 + 2*(3-2) = 8+2 = 10$

c) The question states that we have only a single size RCA. As a result, we know that $k=N/j$, where k = bits of RCA, j = number of blocks.

We can then plug this in to the CSA delay equation to solve for k :

$$2k + 2(N/k) - 4$$

We have the smallest delay when the RCA and MUX delays are approximately equal, so we can rewrite this as:

$$2k = 2(N/k) \rightarrow k = \sqrt{N}$$

For this question, $N=64$, so $k=8$.

Going back to $k=N/j$, solving for j gives $j=8$ as well.

With 8 stages, we have a total of 15 RCAs: one for the first state + 2 for the rest of the stages.

$$1+2*7=15 \text{ RCAs}$$

$$\text{Delay} = 2*8 + 2(8-2) = 16+12 = 28$$

3. [Sequential Timing]

- a) 32 cycles, each with a 64-bit RCA, ignoring shift = $32 * 128 = 4096$ cycles
- b) 32 cycles, each with a 32-bit RCA, ignoring shift = $32 * 64 = 2048$ cycles

4. [Multiplication]

this is similar to the previous question, except that P&H make different assumptions about how the operations are implemented. Please note that for the hardware version, #2 above is more realistic.

P&H solution: For hardware, it takes 1 cycle to do the add, 1 cycle to do the shift, and 1 cycle to decide if we are done. So the loop takes $(3 * A)$ cycles, with each cycle being B time units long.

For a software implementation, it takes 1 cycle to decide what to add, 1 cycle to do the add, 1 cycle to do each shift, and 1 cycle to decide if we are done. So the loop takes $(5 * A)$ cycles, with each cycle being B time units long.

$$(3*8)*4tu = 96 \text{ time units for hardware}$$

$$(5*8)*4tu = 160 \text{ time units for software}$$

5. [Multiplication]

- a) Unrolled using RCAs: Delay = $2N + 4(N-2) \approx 6N$
- b) Unrolled using CSAs: Delay = $2N + 2(N-2) \approx 4N$
- c) Unrolling is faster because it doesn't require row A to be fully computed for row $A+1$ to begin computation while a shift-and-add multiplier does.

6. [Multiplication]

Regardless of how you change the CSA-based multiplier, the timing is not affected.

7. [Floating Point]

3.23 $63.25 \times 10^0 = 111111.01 \times 2^0$

normalize, move binary point 5 to the left

1.1111101×2^5

sign = positive, exp = $127 + 5 = 132$

Final bit pattern: 0 1000 0100 1111 1010 0000 0000 0000 000

= 0100 0010 0111 1101 0000 0000 0000 0000 = 0x427D0000

8. [Floating Point]

- a) 0|0001|0000
- b) 0|1110|1111
- c) 0|0111|0001
- d) 0|0110|1111
- e) 0|1101|1010
- f) 0|1111|0000
- g) 0|1000|0101
- h) 0|0110|1110
- i) 0|1000|0001